

S.V.NATIONAL INSTITUTE OF TECHNOLOGY-SURAT

B. Tech. II (EC) SEM IV

Supplementary End Sem. Exam. July 2013

Electronic Circuits

Marks: 50

Time: 2 hour

Instructions:

1. Attempt all questions.
2. Draw neat & clean circuit diagram/block diagram and waveforms.
3. Figure to the right indicates full marks.
4. Assume data if necessary with proper justification.
5. For Q.5/6/7 take: For n-p-n transistor: $V_{BE(Active)}=0.7V$, $V_{CE(sat.)}=0.2V$, $V_{BE(sat.)}=0.8V$, $V_T=0.6V$
For p-n-p transistor: $V_{BE(Active)}=-0.7V$, $V_{CE(sat.)}=-0.2V$, $V_{BE(sat.)}=-0.8V$, $V_T=-0.6V$

Q.1(a)	Draw the circuit of a BJT amplifier with all its biasing and essential components.	04
Q.1(b)	Calculate the Miller Capacitance of input of an inverting amplifier.	03
Q.2	Draw qualitatively the frequency response (low & high) of the amplifier in Bode plot showing 3 lower cut-off and 3 higher cut-off frequencies, corresponding 3dB gains, mid band gain and bandwidth.	08
Q.3(a)	For voltage Series feedback amplifier, draw equivalent circuit and obtain expression for input and output resistance R_{if} and R_{of} . Give one Example of voltage Series Feedback amplifier and draw circuit for it.	05
Q.3(b)	Explain principle of operation of phase shift Oscillator in detail. Derive Equation of frequency of oscillation for it.	03
OR		
Q.3(b)	Explain Colpitt's oscillator in detail and also, Derive frequency of oscillation for Same.	03
Q.4(a)	For the feedback amplifier shown in Fig.1., 1. identify topology 2.find input and output circuit	04

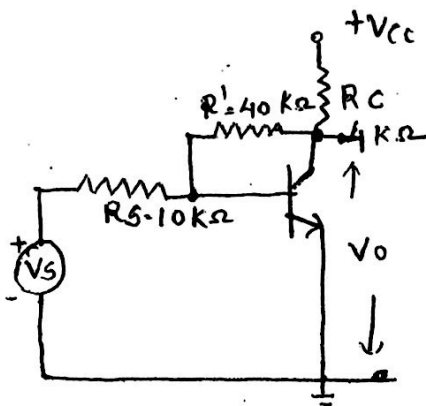


Fig.1

Q.4(b)	In a Colpitt's Oscillator, the values of the inductor and capacitors in the tank circuits are $L=40\text{mH}$, $C_1=100\text{pF}$ and $C_2=500\text{pF}$. 1. Find frequency of oscillations 2. If output voltage is 10V, find feedback voltage 3. Find value of C_1 for gain of 10 4. Find the new frequency of oscillations	03
OR		
Q.4(b)	An Amplifier with open loop voltage gain of 1000 delivers 10W of power output at 10% second harmonic distortion when input is 10mv. If 40dB Desensitivity is given and output power is to remain at 10W. determine required input signal V_s and second harmonic distortion with feedback.	03
Q.5	Derive the expression quasi-stable pulse width for monostable multivibrator	06
Q.6	Design a bistable multivibrator using n-p-n transistors. Neglect I_{CBO} and the voltage drop across collector-to-emitter. Assume $h_{FE\min} = 20$. Take the transistor which is OFF has base-to-emitter voltage of -1V and transistor which is in saturation with a base current 50 percent in excess of its minimum required value. The collector supply and base supply are $V_{cc} = V_{bb} = 10\text{V}$ and the saturated collector current is 5mA.	08
Q.7	Attempt any three:	06
(i)	Define holding current and latching current for thyristor.	
(ii)	Consider self biased bistable multivibrator using p-n-p transistors with $R_1=25\text{K}\Omega$, $R_2=15\text{K}\Omega$, $R_C=5\text{K}\Omega$, $R_E=1\text{K}\Omega$, $C_1=100\text{pF}$, $h_{FE(\min)}=20$, $V_{cc}=-20\text{V}$. Find the maximum frequency of operation.	
(iii)	Consider Astable multivibrator with p-n-p transistors with $V_{cc}=12\text{V}$, $R_C=1.8\text{K}\Omega$, $R_1=10\text{K}\Omega$, $C_1=0.1\mu\text{F}$, $R_2=20\text{K}\Omega$, $C_2=0.01\mu\text{F}$. Find frequency of output voltage.	
(iv)	The compensated attenuator with $V_{cc}=15\text{V}$, $R_1=15\text{K}\Omega$, $C_1=2\mu\text{F}$, $R_2=20\text{K}\Omega$, $C_2=1\mu\text{F}$. Determine $V_{R1}(0^+)$, $V_{R2}(0^+)$, $V_{R1}(\infty)$ and $V_{R2}(\infty)$	
