

**Computer Engineering Department**  
**B. Tech. 2<sup>nd</sup> Year, Semester: 3<sup>rd</sup>**  
**Digital Circuits**  
**Mid Semester Exam- Oct 2013**

**Time: 1 Hour**

**Max. Marks: 30**

**Note:** All Questions are Compulsory.

Design the circuits neatly wherever required.

Sufficient data has been provided, if required assume by your side.

- Q.1** i) Generate the 12 bit even parity Hamming code for 10001011 and at receiver side if code word is 011100110110. find the correct message for odd parity system. **01**
- ii) Perform subtraction using 9's complement method **01**
- a) 20 - 1000      b) 3570 - 2100
- iii) For weighted code 4,4,3,-2 for the decimal digits, determine all possible tables so that 9's complement of each decimal digit is obtained by changing 1's to 0's and 0's to 1's. **02**
- iv) Using 8 bit signed arithmetic perform subtraction using 2's complement method **01**
- a) + 68 - 108      b) + 32 - 49
- Q.2** i) If  $A'B + CD' = 0$  then prove that **02**
- $$AB + C'(A' + D') = AB + BD + B'D' + A'C'D$$
- ii) Reduce Expression using Boolean Theorems ( mention the Theorem applied)
- a)  $(A' + B' + D')(A' + B + D')(B + C + D)(A + C')(A + C' + D) = A'C'D + ACD' + BC'D'$  **02**
- b)  $(A' + B + C')(A' + B + D + E)(C + D)$  **02**
- Q.3** A corporation having 100 shares entitles the owner of each share to cast one vote at the share- holder's meeting. Assume that A has 40 shares, B has 30 shares, C has 20 shares, D has 10 shares. A two third majority is required to pass a resolution in a share holder's meeting. Each of these four men has a switch which he closes to vote YES and opens to vote NO for his percentage of shares. When the resolution is passed the output LED must be ON. Derive a truth table for the output function and give the sum of product equation for it. Also represent the function using NAND- NAND logic. **04**

**P.T.O**


- Q.4 Simplify the Boolean Expression using Mc-Clusky Method  
 $F(A, B, C, D, E, F, g) = \Sigma(20, 18, 38, 39, 52, 60, 102, 103, 127)$   
 Represent the function using NOR-NOR logic.

04

- Q.5 For the sequential circuit shown in Figure below find  
 (a) The state table,  
 (b) The state diagram


04

For 2 bit output AB and 1 bit input X

 

- Q.6 Design sequential circuit for the given state diagram.

04

 

- Q.7 Reduce the number of states in a following state table and tabulate reduced state table for 1 bit input X. Starting from state A determine output sequence for input sequence 10010. The rightmost bits are applied first.

03

Present state	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	C	0	0
B	D	E	0	0
C	F	G	0	0
D	H	I	0	0
E	J	K	0	0
F	L	M	0	0
G	N	P	0	0
H	A	A	0	0
I	A	A	0	0
J	A	A	0	1
K	A	A	0	0
L	A	A	0	1
M	A	A	0	0
N	A	A	0	0
P	A	A	0	0