

Computer Engineering Department
B. Tech. 2nd Year, Semester: 3rd
Digital Circuits
Mid Semester Exam- Sept 2012

Time: 1 Hour

Max. Marks: 30

Note: All Questions are Compulsory.


Design the circuits neatly wherever required.

Sufficient datas have been provided, if required assume by your side.

- Q.1 A) simplify each of the following expression using one of the theorems and state the theorem used. 02
- $(V'W+X)'(V'W+X+Y+Z)$
 - $(V'+W'X)(V'+W'X+Y'Z)$
 - $(W'+X)YZ'+(W'+X)'YZ'$
 - $(V'+U+W)(WX+Y+UZ')+(WX+Y+UZ')$
- B) Octal Subtraction using sign 7's complement and 8's complement method 02
- 1240.70-565.25
 - 520.50-1250.66
- C) Expand to get maxterms and minterms: 02
- $x(x+y')(x'+y+z)$
 - $(w+x')(w'+x'+y)(w+y+z)$
- D) Write function in both SOP & POS form & draw circuits for both the cases. 01
- $F = \prod(0,2,8,9,10,11)+d(12,13,14)$
- Q.2 A Flow rate Sensing device used on a liquid transport pipeline functions as follows. The device 03
- provides a 5-bit output where all five bits are zero if the flow rate is less than 10 gallons per minute. The first bit is 1 if the flow rate is at least 10 gallons per minute; the first and second bits are 1 if the flow rate is at least 20 gallons per minute; the first, second and third bits are 1 if the flow rate is at least 30 gallons per minute and so on. The five bits represented by logic variables A, B, C, D and E are used as inputs to a device that provides two outputs Y and Z.
- Write an equation for the output Y if we want Y to be 1 iff the flow rate is less than 30 gallons per minute.
 - Write an equation for the output Z if we want Z to be 1 iff the flow rate is at least 20 gallons per minute but less than 50 gallons per minute.
- K-Map is required for the mentioned problem.
- Q.3 For each of the following functions find minimum SOP solution using QUINE Mc-CLUSKEY method: 05
- $f(a,b,c,d,e) = \sum m(0,2,3,5,7,9,11,13,14,16,18,24,26,28,30)$
- Q.4 i) Determine that given circuit in figure is a part of combinational logic or sequential logic with 03
- appropriate justification.
-
- ii) "If a clock skew is minimal, flip-flop must be operate reliably." State True/False with appropriate justification.
- iii) What is the difference between state table and excitation table?
- Q.5 For a given 100 MHz clock signal, derive a circuit using D flip-flop to generate 50 MHz & 25 MHz 04
- clock signal. Draw a timing diagram for all three clock signal. Assuming reasonable delays.

 Q.6 The following serial data applied to flip flop shown in figure. Determine the resulting serial data that appears on Q output. Assume there is one clock pulse for each bit time. Assume that Q is initially 0. The rightmost bits are applied first.

J1=10110110 K1=10010110 J2=11011001 K2=11011011



Q.7 Design a sequential circuit using J K flip-flop whose state table is given below:

04

Present State		Input X	Next State		Output Y
A1	A2		A1	A2	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1