

Sardar Vallabhbhai National Institute of Technology

B.Tech. II (CO) 3rd Semester, 2012

Subject: Digital Circuits

End Sem Exam (Dec-2012)


Max. Marks-50

Time 2:00 Hr

Q.1	<p>A Circuit receives a 4- bit Excess-3 code. Find a minimal SOP function for the circuit to detect the decimal nos. 0, 1, 4, 6, 7 and 8. And implement the same using only 2 input NAND gates.</p> <p align="center">OR</p> <p>Design a decimal arithmetic unit with a 9's complements Circuit with two selection variables V1 and V0 and two BCD digits A and B. The unit should have four arithmetic operations which depend on the value of selection variables as shown below. (Note: Using Binary Parallel Adder IC)</p> <table border="0"> <tr> <td>V1</td><td>V0</td><td>OUTPUT</td></tr> <tr> <td>0</td><td>0</td><td>A+9's complement of B</td></tr> <tr> <td>0</td><td>1</td><td>A+B</td></tr> <tr> <td>1</td><td>0</td><td>A+10's complement of B</td></tr> <tr> <td>1</td><td>1</td><td>A+1(add 1 to A)</td></tr> </table>	V1	V0	OUTPUT	0	0	A+9's complement of B	0	1	A+B	1	0	A+10's complement of B	1	1	A+1(add 1 to A)	(05)
V1	V0	OUTPUT															
0	0	A+9's complement of B															
0	1	A+B															
1	0	A+10's complement of B															
1	1	A+1(add 1 to A)															
Q.2	<p>a) Realize given Boolean function $F(W, X, Y, Z) = \sum M(1,2,4,5,9,11,13,14,15)$ using single 8X1 MUX (no enable i/p, selection lines S2 S1 S0= W X Y).</p> <p>b) Construct a 5 X 32 Decoder with four 3X8 Decoders and one 2X4 Decoder (Consider all decoders with Active High I/P , O/P and Enable logic).</p>	(03) (02)															
Q.3	<p>Redefine the carry propagate and carry generate as follows:</p> $P_i = A_i + B_i$ $G_i = A_i B_i$ <p>Show that the output carry and output sum of a full-adder becomes:</p> $C_{i+1} = (C_i' G_i' + P_i)' = G_i + P_i C_i$ $S_i = (P_i G_i') \oplus C_i$	(05)															
Q.4	<p>Hexadecimal-to-seven-Segment decoder is a combinational circuit that accepts hexadecimal digits (0-9 and A-F) in binary (4-bit) and generates appropriate outputs for selection of segments in a display indicator used for displaying a hexadecimal digits. Consider logic 1 required to glow particular segment. Find the functions for a, b, d, e segments using K Map.</p> <div align="center"> </div>	(05)															
Q.5	<p>Design a Binary multiplier that multiplies a 4-bit number $B = b_3b_2b_1b_0$ by a 3-bit number $A = a_2a_1a_0$ to form the product $C = c_6c_5c_4c_3c_2c_1c_0$. This can be done with 12 Gates and two 4-bit parallel adders. The AND gates are used to form the products of pairs of bits. For example, the product of a_0 and b_0. The partial product formed by AND gates are summed with the parallel adders.</p>	(05)															


Answer the following Questions:-

 1. Consider the given circuit. In this circuit, the race around



- [a] does not occur
 [b] Occurs when CLK = 0
 [c] Occurs when CLK = 1 and A = B = 1
 [d] Occurs when CLK = 1 and A = B = 0

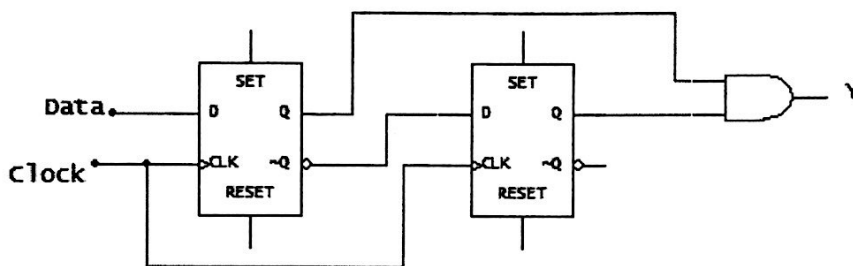
2. When the output Y in the circuit below is "1", it implies that data has



- [a] Changed from "0" to "1"
 [b] Changed from "1" to "0"
 [c] Changed from in either direction
 [d] Not changed

3. The present output Q_n of an edge triggered JK flipflop is logic 0. If $J = 1$, then Q_{n+1}
 [a] cannot be determined [b] will be logic 0 [c] will be logic 1 [d] will race around

 4. The initial contents of the 4 bit serial-in-parallel-out, right-shift, Shift Register shown in figure is 0110. After three clock pulses are applied, the contents of the Shift Register will be





- [a] 0000 [b] 0101 [c] 1010 [d] 1111

5. A 4 bit modulo-16 ripple counter uses JK flipflops. If the propagation delay of each FF is 50 ns, the maximum clock frequency that can be used is equal to:

- [a] 20 MHz [b] 10 MHz [c] 5 MHz [d] 4 MHz

6. State True or False:-

- i) Synchronous data transfer requires less circuitry than asynchronous.
 ii) The CLK input will affect the flip-flop output only when active transition of the control input occurs.

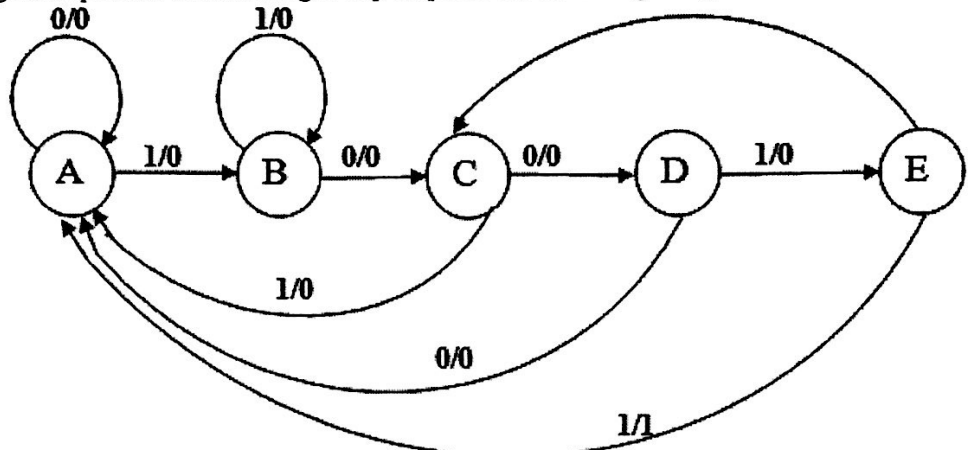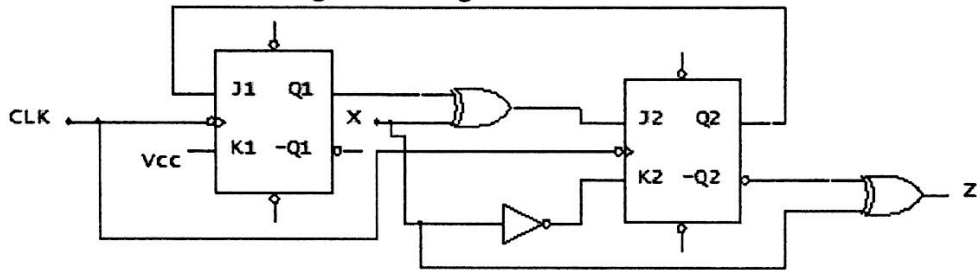Q.7	Explain 4 bit twisted ring counter using D flip-flops with neat logic diagram & waveforms. How can you prevent lock-out condition?	(08)
Q.8	<p>Design a sequential circuit using D flip-flops for the state diagram 0/1 given:</p> 	(05)
Q.9	<p>Obtain the state table & diagram for the given circuit:</p> 	(05)