



S.V. National Institute of Technology, Surat
B.Tech. II (EC), 3rd Semester
Mid Semester Exam, September-2014
Electronic Devices and Circuits (EC201)

Marks: 30

Time: 01Hours

Instructions:

1. Attempt all questions.
2. Draw neat and clean circuit diagram/block diagram and waveforms.
3. **Maintain the Sequence of Answer.**
4. Assume data if necessary with proper justification.

Q.1 Attempt Any One:

06

- (a) List out the different types of biasing methods in BJT. Draw the circuit diagram of fixed bias circuit and derive the equations for all necessary parameters. 06
- (b) Draw the AC equivalent of Common Drain configuration. And derive the equation for voltage gain, input impedance and output impedance. 06

Q.2 Attempt Any Two:

12

- (a) A transistor with $\beta=45$ is used with collector to base resistor R_B biasing with quiescent value of 5V for V_{CE} . If $V_{CC}=24V$, $R_C=10k\Omega$, $R_E=270\Omega$, find the value of R_B (Fig. 1).

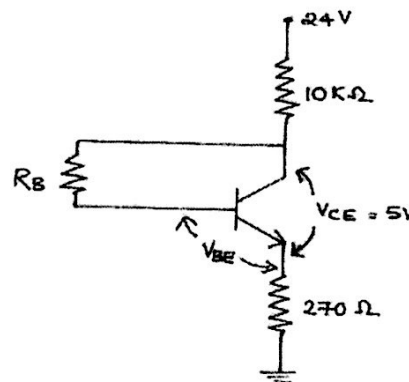


Fig. 1

- (b) For the circuit shown in figure, determine the value of I_C and V_{CE} . Assume $V_{BE}=0.7V$ and $\beta=100$ (Fig. 2).

06

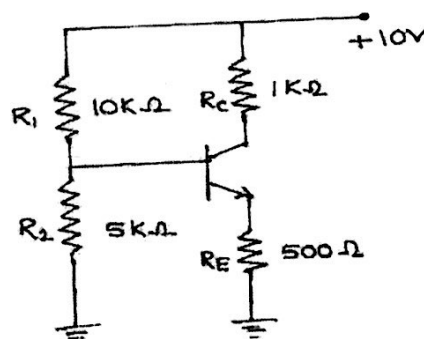


Fig. 2

- (c) Determine V_C and V_B for the circuit diagram shown in Fig. 3.

$$R_C = 1.2 \text{ k}\Omega$$

$$R_S = 100 \text{ k}\Omega$$

$$\beta = 45$$

$$V_{EE} = -9 \text{ V}$$

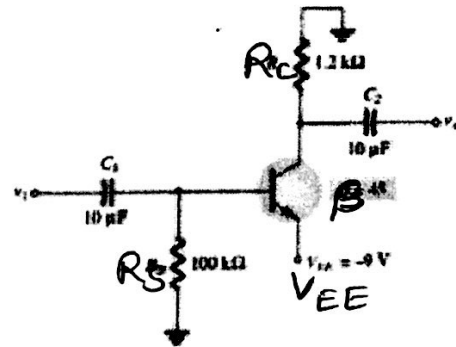


Fig. 3

06

- Q.3 For the network given in Fig. 4, determine : (i) I_{DQ} , V_{GSQ} (ii) V_G , V_D , V_S (iii) Voltage Gain (iv) Input Impedance (v) Output Impedance

$$R_1 = 110 \text{ k}\Omega$$

$$R_2 = 910 \text{ k}\Omega$$

$$R_C = 2.2 \text{ k}\Omega$$

$$R_E = 1.1 \text{ k}\Omega$$

$$I_{DSS} = -10 \text{ mA}$$

$$V_P = -3.5 \text{ V}$$

$$V_{DD} = 20 \text{ V}$$

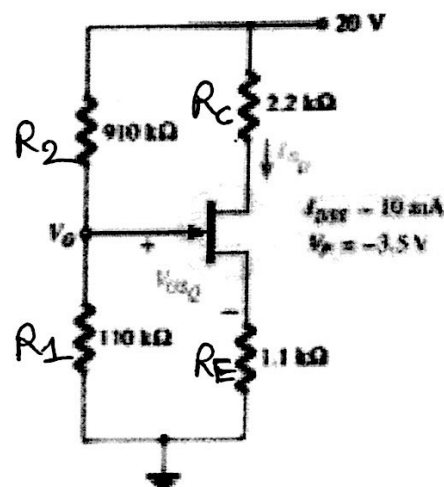


Fig. 4

06

- Q.4 Attempt any Two: (Each 03 marks):

06

For the circuit shown in following Figures explain the working of the circuit, draw the output voltage and the transfer characteristics. In each case assume $V_f = 0$, $R_f = 0$ and $R_r = \infty$.

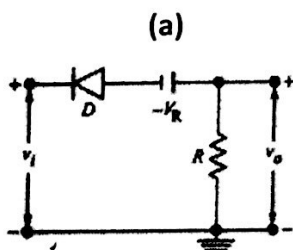


Fig. 5

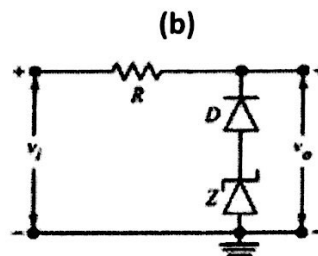


Fig. 6

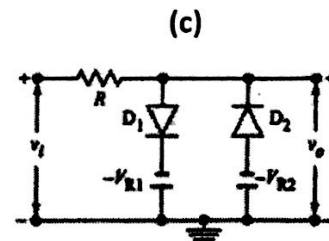


Fig. 7
