

S.V.NATIONAL INSTITUTE OF TECHNOLOGY, SURAT

B. Tech. II (EC) 3rd sem

SUBJECT: Digital Logic Design (EC203)


Mid Test (Sept -2012)

Time: 1 hour

Total Marks: 30

Q.1 a

02

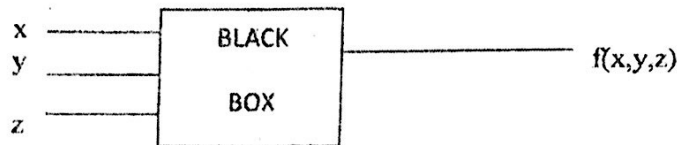


The black box in the above fig. consists of only AND, OR and NOT gates. The function $f(x, y, z) = 1$ wherever x, y are different and 0 otherwise. In addition the 3 inputs x, y, z are never all the same value. Find sum of minterm and Boolean function of $f(x,y,z)$.

- b** Minimize the following Boolean expression in POS form with the help of K-Map : **02**

$$F(u, v, w, x) = \sum m(1, 5, 7, 9, 13) + \sum d(8, 10, 11, 14)$$

- c** Simplify the logic in SOP form for circuit that will cause a light to go on each time the decimal equivalent of a 4 bit binary input is divisible by 3. It is known that the numbers 0,1,7,11,14 will never occur as inputs. Find sum of minterms and product of maxterm also. **03**

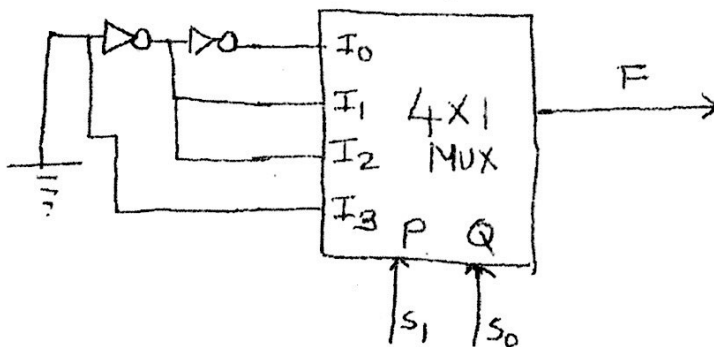- d** What is the function implement at output by following figure? **02**




- e** Write truth table for three coins, where the output is 1 if and only if exactly one of the coins is Head after a toss of three coins at a time. (i) Find the minterm expansion of F. Implement F using active high output decoder. **03**

- f** Design the simplified circuit NOR-NOR realization for the Boolean function **03**

$$ABCD + AB'C'D' + A'B'CD + A'BC'D + ABCD' + A'BCD' + A'BCD$$

OR

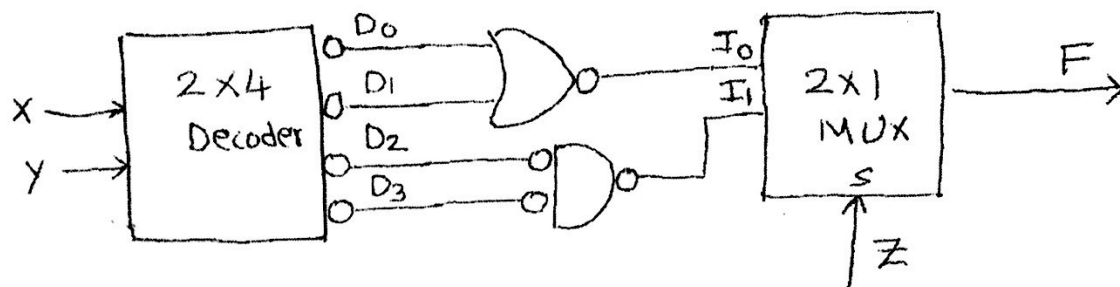- f Find logic value **HIGH/LOW** for I_0 , I_1 and F for following figure if i) $xyz=001$ ii) $xyz=110$ 03




- Q:2 a A person on a SATURN processing 18 fingers has a property worth $(1, 00,000)_{18}$. He has 3 daughters & 2 sons. He wants to distribute half of the money equally to his sons & remaining half to his daughters. How much his each son & each daughter will get in Indian currency? 03
- b The state of 12-bit register is 1000 1001 0111. What is its equivalent value in decimal, if it represents in (i) 8421 BCD code (ii) binary gray code & (iii) 84-2-1 BCD code. 03
- c The 2's complement representation of a 16 sign bit number is FFFF. Represent the magnitude of this number in decimal. 01
- d Express $(-45)_{10}$ in 8 bit sign 2's complement form. 01

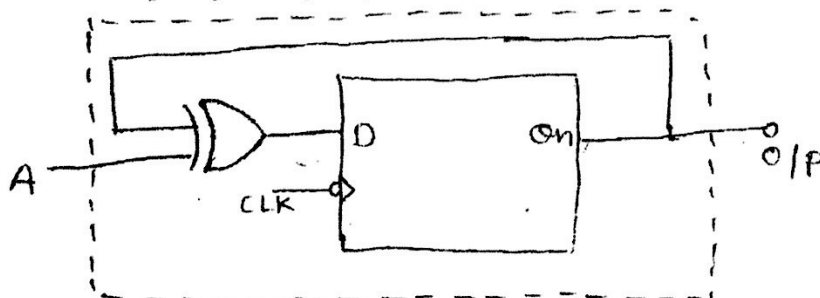Q:3
a

Make the characteristic table and characteristic equation for the following flip-flop, having input A. 03

- Whether the functionality of this flip flop equivalent to any four flip flop? If yes, find which one.
- If $A=1$ and 50 khz clock is applied to this flip flop what will be the frequency of output Q?



- b Realize the sequential circuit for the state diagram shown in fig. Use D flip-flop 04

