

Time: 1Hr.]

[Total Marks: 30

- Q.1 (a) Determine the base of the numbers in LHS for each case of the following operations to be correct: (i) $203/12 = (15)_{10}$ (ii) $24 * 18 = (320)_{10}$ [3]

OR

A particular number system has two consecutive digits X and Y, when written as XY gives decimal value 129 and when written as YX gives decimal value 143. Find the base of this number system and digits X and Y.

- (b) Multiply following numbers without converting to any other base. [3]
 $(135.4)_6 \times (14.4)_6$
- (c) Obtain 2's complement of binary numbers 011010 and 010.010. [2]
- (d) Convert following decimal numbers in to base 5 and base 7. (i) 234.125 (ii) 98.23 [4]


- Q.2 (a) Simplify the Boolean function $F(W,X,Y,Z) = \sum(0,1,2,8,9,11,15)$ that has Don't care as $d(W,X,Y,Z) = \sum(7,4)$ [3]
- (b) Obtain boolean equation of borrow output of a Full Subtractor and realize it with NAND only logic. [3]

OR


Simplify following Boolean expression by algebraic manipulation.

$$f(k,l,m,n) = k'lm' + k'm'n + klm'n' + lmn'$$

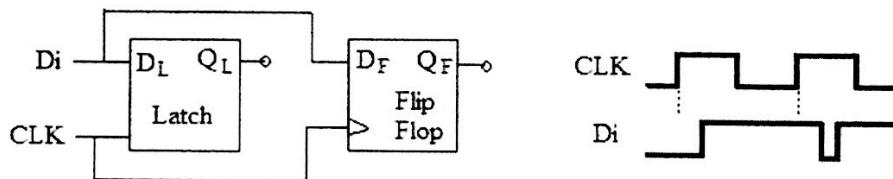- (c) Design Even parity generator for 4-bit message and implement it with two input X-NOR gates and an inverter. [3]
- Q.3 (a) Draw the waveform of output of latch Q_L and output of positive edge triggered flip flop Q_F if both $Q_L = Q_F = 0$ initially. [2]



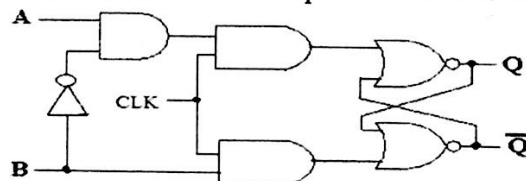- (b) Obtain characteristic table and characteristic equation of following latch. [3]



- (c) Design & Draw clocked sequential circuit for state diagram shown below using JK flip flop. [4]

