

S.V.NATIONAL INSTITUTE OF TECHNOLOGY, SURAT
B. Tech. II (EC) 3rd sem

SUBJECT: Digital Logic Design (EC203)

Mid Test (Sept -2014)

Time: 1 hour

Total Marks: 30

- Q.1 (a)** Convert gray number 10110010 into decimal, BCD, 84-2-1 and EX_3 codes. 02
- (b)** Consider 10 bit register is used to store the numbers. Perform subtraction of - 257 - 169 using sign 1's complement method. 02
- (c)** Perform subtraction of $(342.7)_{10} - (108.9)_{10}$ in BCD code using 10's complement method. 03
- (d)** $(12)_x + (81)_x = (77)_x$ then find its radix x. 01
- Q 2 (a)** Convert SR flip-flop into T flip-flop. 02
- (b)** A sequential circuit has one input x and its state diagram is shown in figure.1. Design the sequential circuit using positive edge trigger JK flipflops. 04

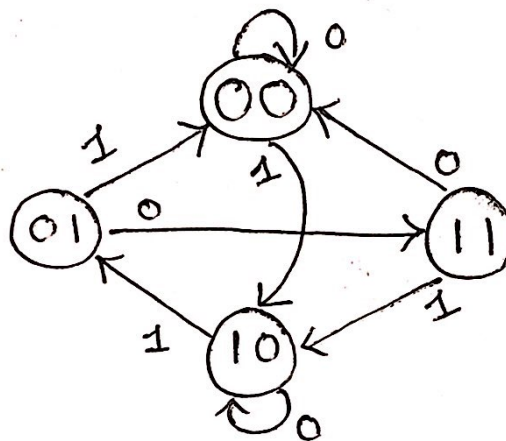


Fig. 1

- (c)** Consider Boolean function $F(A,B,C,D) = \sum m(2,8,9,13,14)$. It's simplified SOP is $B'D' + CD' + AC'D$. Are there any don't care numbers? If so what are they numbers? 02
- OR**
- (c)** For the logic circuit shown in figure 2, what is the required input condition to make the output 1? 02

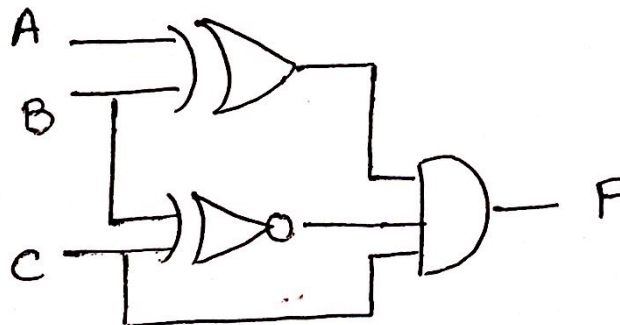


Fig. 2

Q 3 (a) Design single bit magnitude comparator using only 2 input NAND gates. 04

(b) Design a circuit with three inputs A,B ,C and two outputs X and Y. The output X is HIGH if and only if total number of 1 in input are odd. The output Y is HIGH whenever at least two inputs are 1. Write down truth table. Find simplified circuit diagram. 04

(c) For the following figure 3 find 03
 i) Boolean expression for Y
 ii) Boolean expression for X and sum of minterms for X(A,B,C).

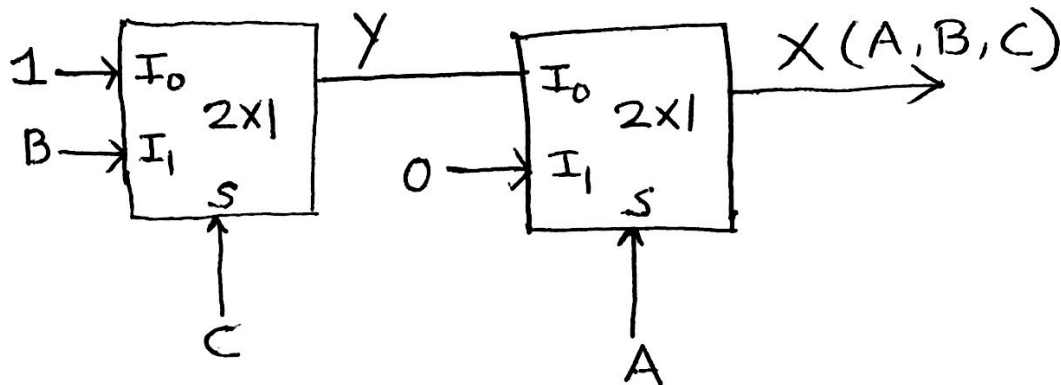


fig : 3

(d) For the following figure 4 find HIGH/LOW for I_0, I_1 and Y if EWXYZ=10010, 00011, 01011. 03

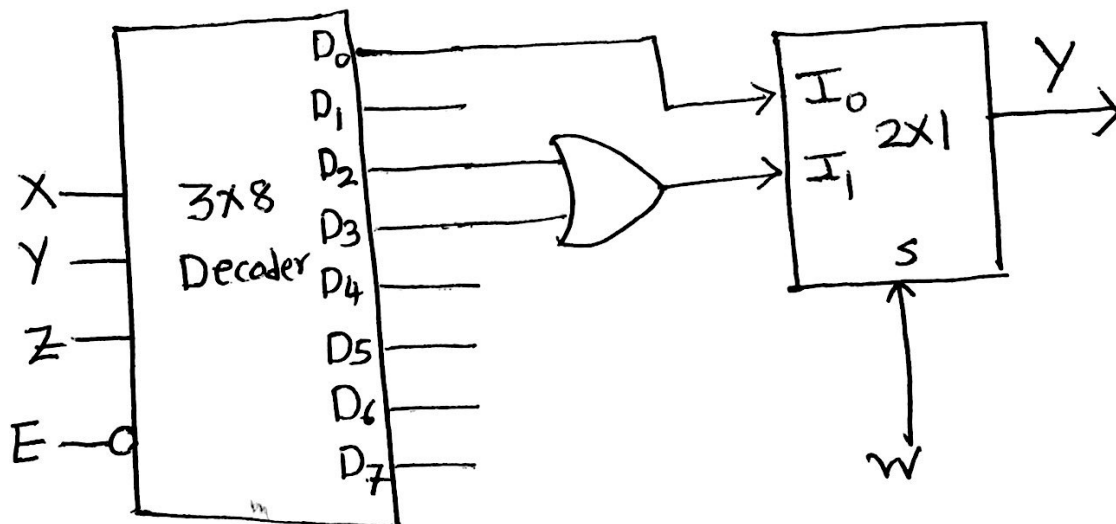


fig : 4
